

Andy Jeong, Brenda So, Gordon Macshane

ECE 151A

Spring 2016

22 February 2016


Project 1: Paper Processor

Abstract

This project aims to construct a circuit on Verilog Hardware Description Language whereby the paper processor (https://sites.google.com/site/kotukotuzimiti/Paper_Processor) is implemented. The Verilog code takes in the modules (.v) – *checking*, *dff*, *dfff*, *halt*, *increment*, *jno*, *programcounter*, *two_bit_fa*, *twoBitRam* – which take the inputs and outputs the data bits according to the logic gates event-driven cases (*jno*) and delays.

Diagram (refer to *waveform.png*)

 Waveform 1: Paper Processor implementation for time duration = 82 (ns)



Compiling and Running the Code (refer to *Build.txt*)

To compile on terminal:

```
iverilog -o <objectname> main_tb.v
```

To run the compiled object file:

```
vvp <objectname>
```

To see the waveform using GTKWAVE simulator (as defined in code as "pp.vcd"):

```
gtkwave pp.vcd
```

To remove the object file:

```
rm <objectname>
```

Paper Processor Design (refer to *program.asm*)*The Paper Processor Instructions*

Inc	//increments the address, register
jno 00 ₍₂₎	//jump if not overflow
hlt	//halt
nop	//no operation

Verilog Code*Main Testbench Code (refer to *main_tb.v*)*

```

`timescale 1ns / 1ns

`include "twoBitRam.v"
`include "increment.v"
`include "programcounter.v"
`include "halt.v"
`include "jno.v"
`include "checking.v"
`include "dff.v"
`include "dfff.v"

module main_tb();

    reg status;                                // status register
    reg clock;                                // clock register
    wire monostable;                          // monostable clock induced by inc
    logic
    wire pulse;                                // clock induced
    by halt
    wire monostabler;
    reg [1:0] out;                            // output registers
    wire w3, w4, w5, w6;
    wire openpulser;                          //Pulse from JNO, imitating
    monostable timer

    reg [1:0] constant;                       // INC logic: add to full adder
    wire [1:0] adder_to_out;                  // INC logic :connect adder to reg out
    wire adder_to_stat;                       // ING logic: ddding to
    status
    wire [1:0] instruct;                      // output instruction from RAM
    (LSB)
    wire [1:0] instructA;                    // actual instruction after
    checking
    reg [1:0] Resetter;                      //used to initialize the
    program counter

```

```

wire enabled, enabled_sta;
wire [1:0] PC;                                     // Counter: program counter
output

initial begin

    //print out things to monitor
    $monitor ("time = %g\t PC = %b instruct = %b out = %b stat = %b", $time, PC,
instruct, out, status);

    clock = 0;                                     // initialize clock to be 0
    status = 0;                                     // initialize status to be 0

    out[0] = 0;                                     // initialize LSB to be 0
    out[1] = 0;                                     // initialize MSB to be 0
    constant[0] = 1;                               // constant added to adder
    constant[1] = 0;                               // constant added to adder
    Resetter[1] = 0;
    Resetter[0] = 0;

    #1 Resetter[1] = 1;
    Resetter[0] = 1;
    #1 Resetter[1] = 0;
    Resetter[0] = 0;
    //let the simulation run for 15 seconds
    #80 $finish;
end

initial begin
    $dumpfile ("pp.vcd");    //for waveform file in .vcd format
    $dumpvars;
end

//only when the instructions are 00
always @(posedge monostabler)
begin
    out[0] <= adder_to_out[0];
    out[1] <= adder_to_out[1];
end

//set the status such that once the status turns 1 it would never change back
//to zero
always @(posedge monostabler)
begin
    status <= adder_to_stat;
end

//Set the clock to alter every second

```

```

always begin
    #4 clock = ~clock; // Generate clock
end

//Connect twoBitRam to test bench

twoBitRam raml(
    PC,
    instruct
);

//connect increment blackbox to testbench
increment inc(
    adder_to_out,
    adder_to_stat,
    monostable,
    out,
    instructA);

//connect counter to testbench
programcounter pc(
    PC,
    openpulser,
    Resetter,
    instruct,
    pulse,
    enabled_sta);

and (monostabler, monostable, !status);

//connect halt blackbox to program counter
halt hlt(
    pulse,
    clock,
    instructA);

//connect jno blackbox to checking logic
jno jnoo(enabled, enabled_sta, openpulser, status, instructA, pulse);
checking checkers(instructA, enabled, instruct);

endmodule

```

checking.v (refer to *checking.v*)

```
`timescale 1ns / 1ns
```

```

module checking(checked, enabling, check);

//-----Input Ports-----

input [1:0] check;      //input a 2 bit register from JNO
input enabling;

//-----Output Ports-----

output [1:0] checked;

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] check;
wire enabling;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire [1:0] checked;

//-----Intermediate Wires-----

//-----Instructions-----

or o1(checked[1], enabling, check[1]);
or o2(checked[0], enabling, check[0]);

endmodule

```

dffr.v (refer to dff.v)

```

`timescale 1ns / 1ns

module dff (clk, s, r, d, q, qbar);
    input clk, s, r, d;
    output q,qbar;
    reg q,qbar;
    always @(negedge r) begin
        q = 1'b0;
        qbar = 1'b1;
    end
    always @(negedge s) begin
        q = 1'b1;
        qbar = 1'b0;
    end
end

```

```

        always @(posedge clk) begin
            #1
            q = d;
            qbar = ~d;
        end

endmodule

```

dfff.v (refer to *dfff.v*)

```

`timescale 1ns / 1ns

module dfff (clk, s, r, d, q, qbar);
    input clk, s, r, d;
    output q, qbar;
    reg q, qbar;
    always @(posedge r) begin
        q = 1'b0;
        qbar = 1'b1;
    end
    always @(posedge s) begin
        q = 1'b1;
        qbar = 1'b0;
    end
    always @(posedge clk) begin
        #1
        q = d;
        qbar = ~d;
    end

endmodule

```

halt.v (refer to *halt.v*)

```

`timescale 1ns / 1ns

module halt(pulses, clk, instruct);

//-----Input Ports-----

input [1:0] instruct;    //input a 2 bit register from JNO
input clk;

//-----Output Ports-----

output pulses;

//-----Input ports Data Type-----

```

```
// By rule all the input ports should be wires
wire [1:0] instruct;
wire clk;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire pulses;

//-----Intermediate Wires-----
wire w1;
wire w2;

//-----Instructions-----

and a1(w1, instruct[1], !instruct[0]);
not n1(w2, w1);

and(pulses, clk, w2);

endmodule
```

increment.v (*refer to increment.v*)

```
`timescale 1ns / 1ns

`include "two_bit_fa.v"

module increment(value, sta, mn, prev_value, instruct);

//-----Input Ports-----

input [1:0] instruct;     //input a 2 bit register from JNO
input [1:0] prev_value;

//-----Output Ports-----

inout [1:0] value;
output sta;
output mn;

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] instruct;
wire [1:0] clk;
wire [1:0] prev_value;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
```



```

wire [1:0] value;
wire sta;
wire mn;

//-----Intermediate Wires-----

//-----Instructions-----

and (mn, !instruct[1], !instruct[0]);
fulladder adder(sta, value, prev_value);

endmodule

```

jno.v (refer to *jno.v*)

```

`timescale 1ns / 1ns

module jno(enabling, enabling_sta, openpulse, sta, instruct, pulses);

//-----Input Ports-----

input [1:0] instruct;    //input a 2 bit register from JNO
input pulses;
input sta;

//-----Output Ports-----

output enabling;
output enabling_sta;
output openpulse;

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] instruct;
wire pulses;
wire sta;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire enabling;
wire enabling_sta;

//-----Intermediate Wires-----
reg s;
reg r;
wire notenabling, notenabling_sta;

```

```

wire w1, w2;
reg mem;
reg pulser;
wire openpulse;
reg openpulser;

//-----Instructions-----
initial begin
s = 0;
r = 0;
pulser = 0;
openpulser = 0;
end

and a1(w1, !instruct[1], instruct[0]);
and a2(w2, !sta, !instruct[1], instruct[0]);
and a3 (openpulse, !sta, openpulser);

always @(posedge w1)
begin
    #1
    pulser = 1;
    #8
    openpulser = 1;
    #4
    openpulser = 0;
    #1
    pulser = 0;
    #1
    pulser = 1;
    #1
    pulser = 0;

end
dff dff3(pulser, s, r, w1, enabling, notenabling);           //enabling
the checking
dff dff4(pulser, s, r, w2, enabling_sta, notenabling_sta);    //enabling for counter

endmodule

```

programcounter.v

(refer to programcounter.v)

```

`timescale 1ns / 1ns

module programcounter(select, openpulse, R, jno, clk, enabled);

//-----Input Ports-----

input [1:0] jno;           //input a 2 bit register from JNO

```

```

input clk;                      //input clock signal
input enabled;                  //input enabling JNO register addresses
input [1:0] R;                  //for resetting
input openpulse;

//-----Output Ports-----

output [1:0] select;

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] jno;
wire clk;
wire enabled;
wire [1:0] R;
wire openpulse;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire [1:0] select;

//-----Intermediate Wires-----

wire [1:0] selectN;
wire w1, w2,w3,w4, w5, w6;
wire [1:0] D;
wire [1:0] S;
wire [1:0] R_temp;

//-----Instructions-----
and a1(S[0], openpulse, enabled, jno[0]);
and a2(S[1], openpulse, enabled, jno[1]);
and a3(w3, openpulse, enabled, !jno[0]);
and a4(w4, openpulse, enabled, !jno[1]);
or o1(R_temp[0], w3, R[0]); //R[0] is 0, w1 goes from 0 to 1
or o2(R_temp[1], w4, R[1]); //

dff0 dff0(clk, S[0], R_temp[0], D[0], select[0], selectN[0]);
dff1 dff1(clk, S[1], R_temp[1], D[1], select[1], selectN[1]);

and (w1, selectN[0], select[1]);
and (w2, selectN[1], select[0]);
or (D[1], w1, w2);
and (D[0], selectN[0],1);

endmodule

```

two_bit_fa.v (refer to *two_bit_fa.v*)

```
`timescale 1ns / 1ns

module fulladder(stat, sum, a);

//-----Input Ports-----

inout [1:0] a; //input a 2 bit register

//-----Output Ports-----

output [1:0] sum; //output 2 bit registers
output stat; //see whether registers overflowed

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] a;
wire [1:0] b;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire [1:0] sum;
wire stat;

//-----Intermediate Wires-----
wire w0, w1, w2, w3, w_sum0, w_sum1, w_stat;

//-----Instructions-----
//set LSB of input to w_sum0
xor u0(w_sum0,a[0], 1'b1);
and (sum[0], w_sum0, 1);

//set MSB of input to w_sum1
and u1(w0, a[0], 1'b1);
xor u2(w1, a[1], 1'b0);
and u3(w2, a[1], 1'b0);
and u4(w3, w0, w1);
xor u5(w_sum1, w0, w1);
and(sum[1], w_sum1,1);

//set carry out to be w_stat
or u6(w_stat,w2, w3);
and (stat, w_stat,1);

endmodule
```

twoBitRam.v (refer to *twoBirRam.v*)

```

`timescale 1ns / 1ns

module twoBitRam(addr, data);

//-----Input Ports-----

input [1:0] addr;

//-----Output Ports-----

output [1:0] data;

//-----Input ports Data Type-----
// By rule all the input ports should be wires
wire [1:0] addr;

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
wire [1:0] data;

//-----Instructions-----
/*
Instructions:
INC: 00
JNO: 01
HLT: 10

in1: INC
in2: JNO
in3: 00
in4: HLT
*/

//First Demux
and and1_msb(a1_msb, !addr[1], !addr[0], 1'b0);
and and2_msb(a2_msb, !addr[1], addr[0], 1'b0);
and and3_msb(a3_msb, addr[1], !addr[0], 1'b0);
and and4_msb(a4_msb, addr[1], addr[0], 1'b1);

//Second Demux
and and1_lsb(a1_lsb, !addr[1], !addr[0], 1'b0);
and and2_lsb(a2_lsb, !addr[1], addr[0], 1'b1);
and and3_lsb(a3_lsb, addr[1], !addr[0], 1'b0);
and and4_lsb(a4_lsb, addr[1], addr[0], 1'b0);

//Final Or Gate
or or_msb(data[1], a1_msb, a2_msb, a3_msb, a4_msb);
or or_lsb(data[0], a1_lsb, a2_lsb, a3_lsb, a4_lsb);

```

```
endmodule
```

Sample Output (refer to sample_output.txt)

VCD info: dumpfile pp.vcd opened for output.

```
time = 0    PC = xx instruct = xx out = 00 stat = 0
time = 1    PC = 00 instruct = 00 out = 01 stat = 0
time = 5    PC = 01 instruct = 01 out = 01 stat = 0
time = 13   PC = 10 instruct = 00 out = 01 stat = 0
time = 14   PC = 00 instruct = 00 out = 01 stat = 0
time = 21   PC = 01 instruct = 01 out = 10 stat = 0
time = 29   PC = 10 instruct = 00 out = 10 stat = 0
time = 30   PC = 00 instruct = 00 out = 10 stat = 0
time = 37   PC = 01 instruct = 01 out = 11 stat = 0
time = 45   PC = 10 instruct = 00 out = 11 stat = 0
time = 46   PC = 00 instruct = 00 out = 11 stat = 0
time = 53   PC = 01 instruct = 01 out = 00 stat = 1
time = 61   PC = 10 instruct = 00 out = 00 stat = 1
time = 69   PC = 11 instruct = 10 out = 00 stat = 1
```